

CET 323 LAB

Name Van Nguyen

Dr. Park

Date September 25, 2020.

Class CET 323\_01

## FET Amplifiers And Switching Circuits

### Reading

Floyd, Electronic Devices, Ninth Edition, Chapter 9.

### Key Objectives

Part 1 : Calculate and measure dc and ac parameters for a common-Source amplifier.

Part 2 : Calculate and measure dc and ac parameters for two common-drain amplifiers.

### Components need

Part 1 : The common-Source JFET amplifier.

Resistor (one of each) :  $620\ \Omega$  ,  $1.0\ \text{k}\Omega$  ,  $3.3\ \text{k}\Omega$  ,  $10\ \text{k}\Omega$  ,  $100\ \text{k}\Omega$  ,  $1.0\ \text{M}\Omega$

One 2N5484 n-channel JFET.

Capacitors (one if each):  $0.1\ \mu\text{F}$  ,  $1.0\ \mu\text{F}$  ,  $10\ \mu\text{F}$

Part 2 : The common-Drain JFET amplifier.

Resistor (one of each) :  $470\ \Omega$  ,  $1.0\ \text{k}\Omega$  ,  $10\ \text{k}\Omega$  ,  $100\ \text{k}\Omega$  ,  $1.0\ \text{M}\Omega$

One 2N5484 n-channel JFET.


Capacitors (one if each):  $0.1\ \mu\text{F}$  ,  $1.0\ \mu\text{F}$  ,  $10\ \mu\text{F}$

### Part 1 : The common-Source JFET amplifier

1. Measure and record the values of the resistor listed in the Table 9\_1
2. Construct the common-source (CS) amplifier shown in Figure 9\_1. Set the signal generator for a 500 mV<sub>pp</sub> sine wave at 1.0 kHz. Check the amplitude and frequency with your oscilloscope.

**Table 9\_1**

Resistor	Listed Value	Measured Value
$R_S$	1.0 k $\Omega$	
$R_D$	3.3 k $\Omega$	
$R_G$	1.0 M $\Omega$	
$R_L$	10 k $\Omega$	

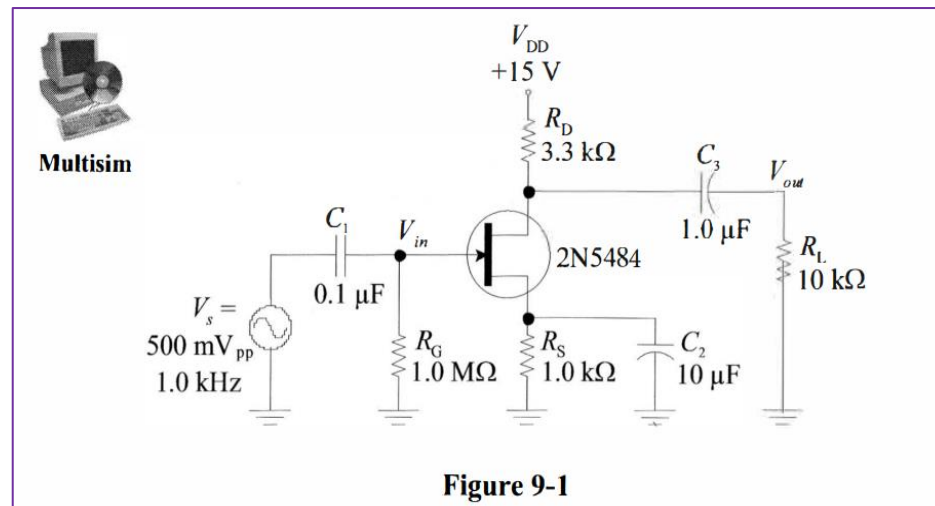


3. Measure the dc voltages listed in Table 9\_2 and compute  $I_D$ . Set the function generator for a 500 mVpp sine wave and measure the ac quantities listed. Compare the input and output ac voltage by viewing  $V_{in}$  and  $V_{out}$  simultaneously. Measure the voltage gain and note the phase different ( $0^\circ$  or  $180^\circ$ ) between the input and output signal. Enter all from this step in Table 9\_2.

**Table 9\_2 Parameters for CS Amplifier**

Quantity	DC value	AC value
Gate Voltage, $V_G$		
Source Voltage, $V_s$		
Drain Voltage, $V_D$		
Drain Current, $I_D$		
Input Voltage, $V_{in}$		
Output Voltage, $V_{out}$		
Voltage gain, $A_v$		
Phase difference		



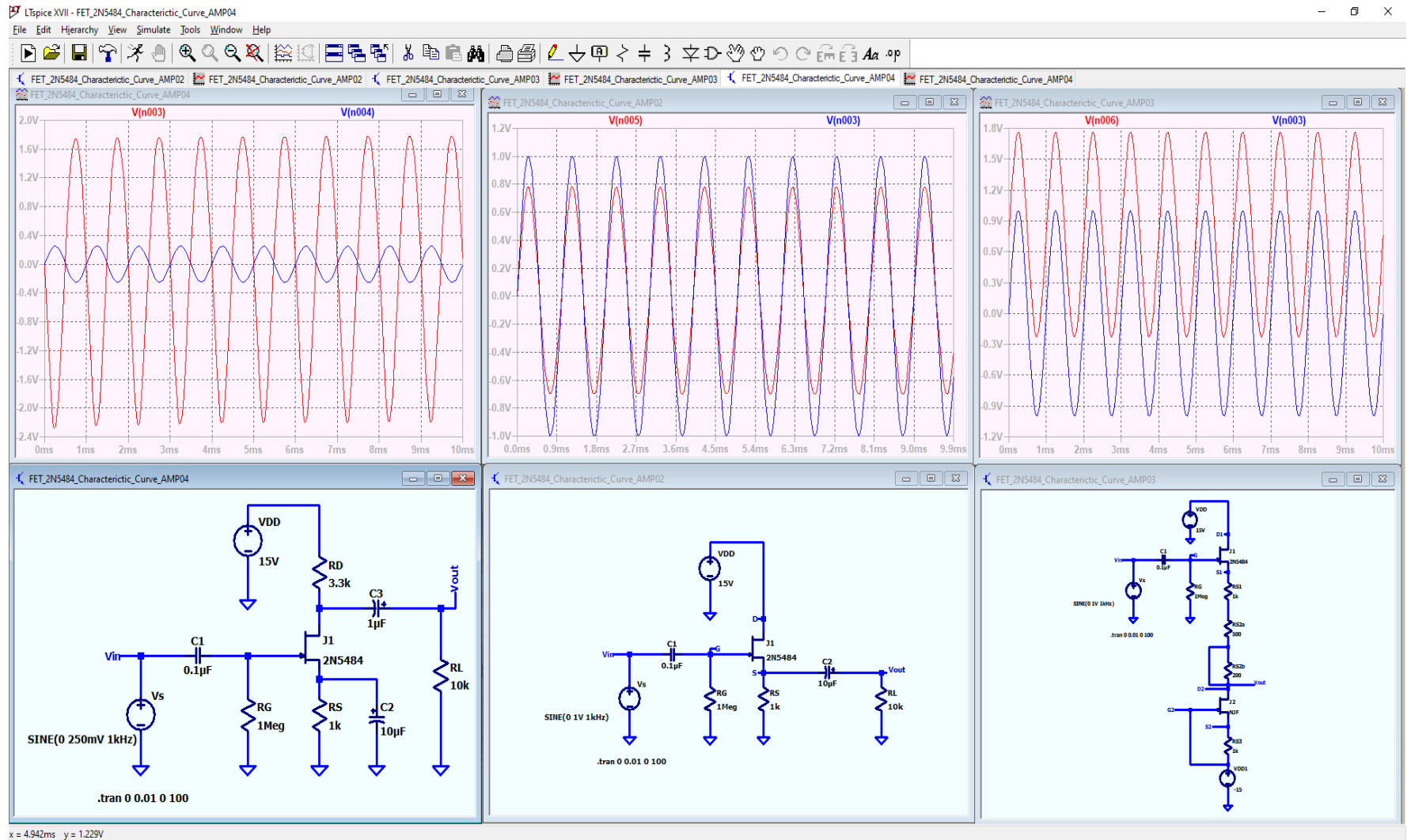

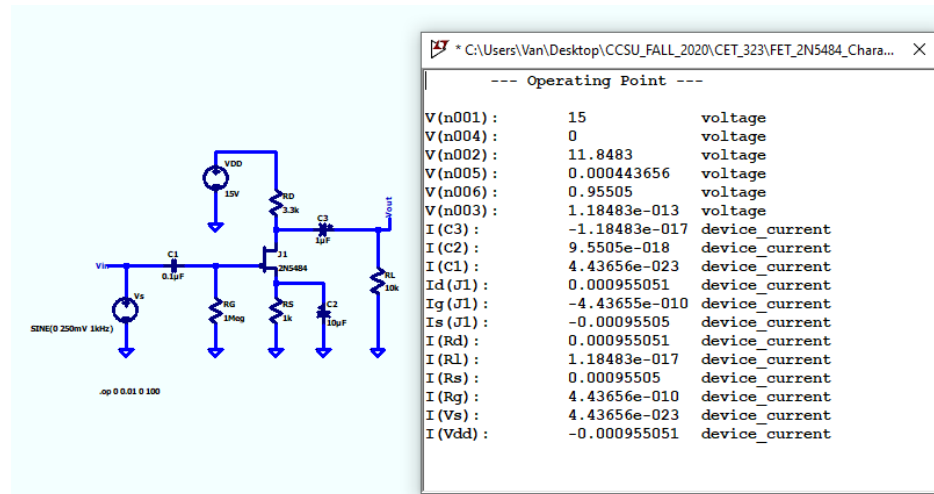



Table 9\_2 Parameters for CS Amplifier

Quantity	DC value	AC value
Gate Voltage, $V_G$ (n005)	0.44 $\mu$ V	
Source Voltage, $V_s$ (n006)	0.955 V	
Drain Voltage, $V_D$ (n001)	15V	
Drain Current, $I_D$ ( $V_{dd}$ )	-0.96 kA	
Input Voltage, $V_{in}$ (n004)		0
Output Voltage, $V_{out}$ (n003)		1.1483e V
Voltage gain, $A_v$		
Phase difference		

```

C:\Users\Van\Desktop\CCSU_FALL_2020\CET_323\FET_2N5...
--- Operating Point ---
V(n001):      15          voltage
V(n003):      0          voltage
V(n002):      0.00346412  voltage
V(n004):      0.963183   voltage
V(n005):      9.63183e-014 voltage
I(C2):        -9.63183e-018 device_current
I(C1):        3.46412e-022 device_current
Id(J1):       0.000963186 device_current
Ig(J1):       -3.46412e-009 device_current
Is(J1):       -0.000963183 device_current
I(R1):        9.63183e-018 device_current
I(Rs):        0.000963183 device_current
I(Rg):        3.46412e-009 device_current
I(Vs):        3.46412e-022 device_current
I(Vdd):       -0.000963186 device_current

```

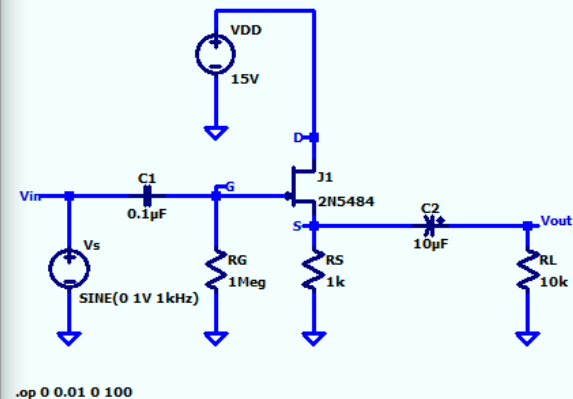

**Table 9\_2 Parameters for CS Amplifier**

Quantity	DC value	AC value
Gate Voltage, $V_G$ (n002)	3.46 kV	
Source Voltage, $V_s$ (n004)	0.963 V	
Drain Voltage, $V_D$ (n001)	15 V	
Drain Current, $I_D$ (Vdd)	- 0.963 $\mu$ A	
Input Voltage, $V_{in}$ (n003)		0
Output Voltage, $V_{out}$ (n005)		9.63183e
Voltage gain, $A_v$		
Phase difference		

**Table 9\_2 Parameters for CS Amplifier**

Quantity	DC value	AC value
Gate Voltage, $V_G$ (n002)	1.06 kV	
Source Voltage, $V_s$ (n004)	1.20578 V	
Drain Voltage, $V_D$ (n001)	15 V	
Source Voltage, $V_{s1}$ (n005)	0.913984 V	
Source Voltage, $V_{s2}$ (n008)	-14.7 V	
Gate Voltage, $V_{G2}$ (n007)	- 15 V	
Drain Current , $I_D$ (Vdd)	-0.291797 $\mu$ A	
Input Voltage, $V_{in}$ (n003)		0 V
Output Voltage, $V_{out}$ (n006)		0.768086 V
Voltage gain, $A_v$		
Phase difference		

