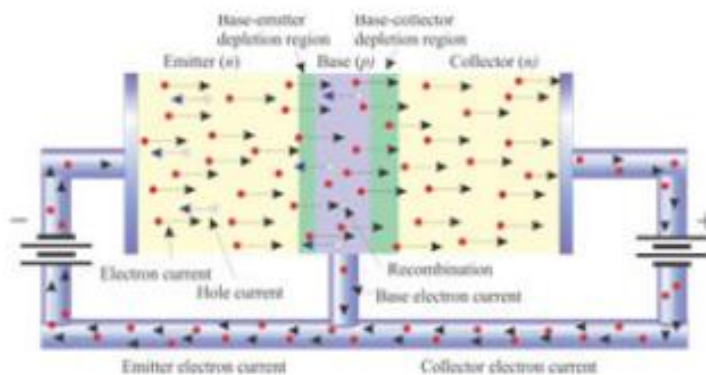




Chapter 15_ LAB_ 11 REPORT_Active Filters SIMULATION

2-pole & 4 -pole



To : Professor . Dr. Park Sangho
Computer engineering Technology

From: Van Thi Minh Nguyen

CET 323_01 CRN: 11342


December 10th , 2020

---***---

LAB_11**Active Filters SIMULATION****Reading**

Floyd, Electronic Devices, Ninth Edition, **Chapter 15. Active Filters**

Basic filter responses are:

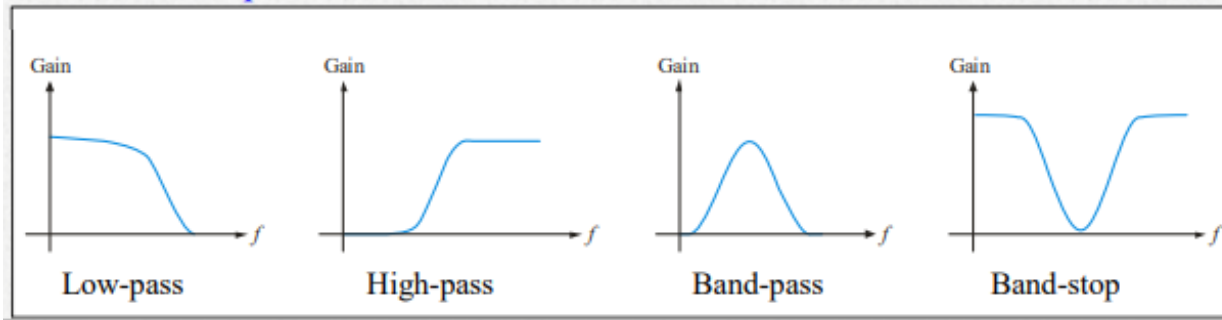

- ❖ In this lab, you will implement and simulate the following two filters using Sallen-Key filter configurations involving RC pairs
- 2-pole Low-pass Butterworth filter
- 4-pole High-pass Butterworth filter

The Damping Factor

Parameters for **Butterworth filters** up to four poles are given in the following table. (See text for larger order filters).

Butterworth filter values

Order	Roll-off dB/decade	1 st stage			2 nd stage		
		Poles	DF	R_1/R_2	Poles	DF	R_1/R_2
1	-20	1	Optional				
2	-40	2	1.414	0.586			
3	-60	2	1.00	1.00	1	1.00	1.00
4	-80	2	1.848	0.152	2	0.765	1.235


Notice that the gain is 1 more than this resistor ratio. For example, the gain implied by this ratio is 1.586 (4.0 dB).



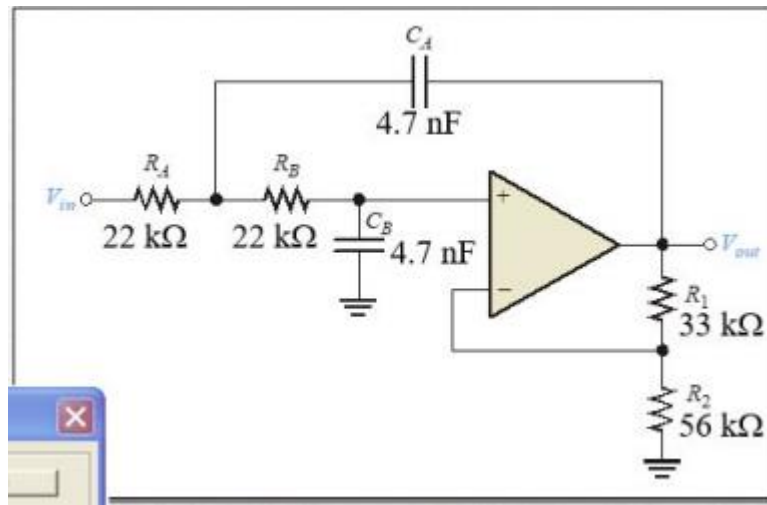Part 1 : Low-Pass Butterworth filter.

- Implement 2-pole Low-Pass Butterworth filter:


Two pole 2-pole Low Pass Butterworth Design



- 1)- Calculate critical frequency.


$$f_c = \frac{1}{2\pi RC} = \frac{1}{2(3.1416)(1 \text{ k}\Omega)(1 \text{ }\mu\text{F})} = 159 \text{ Hz}$$

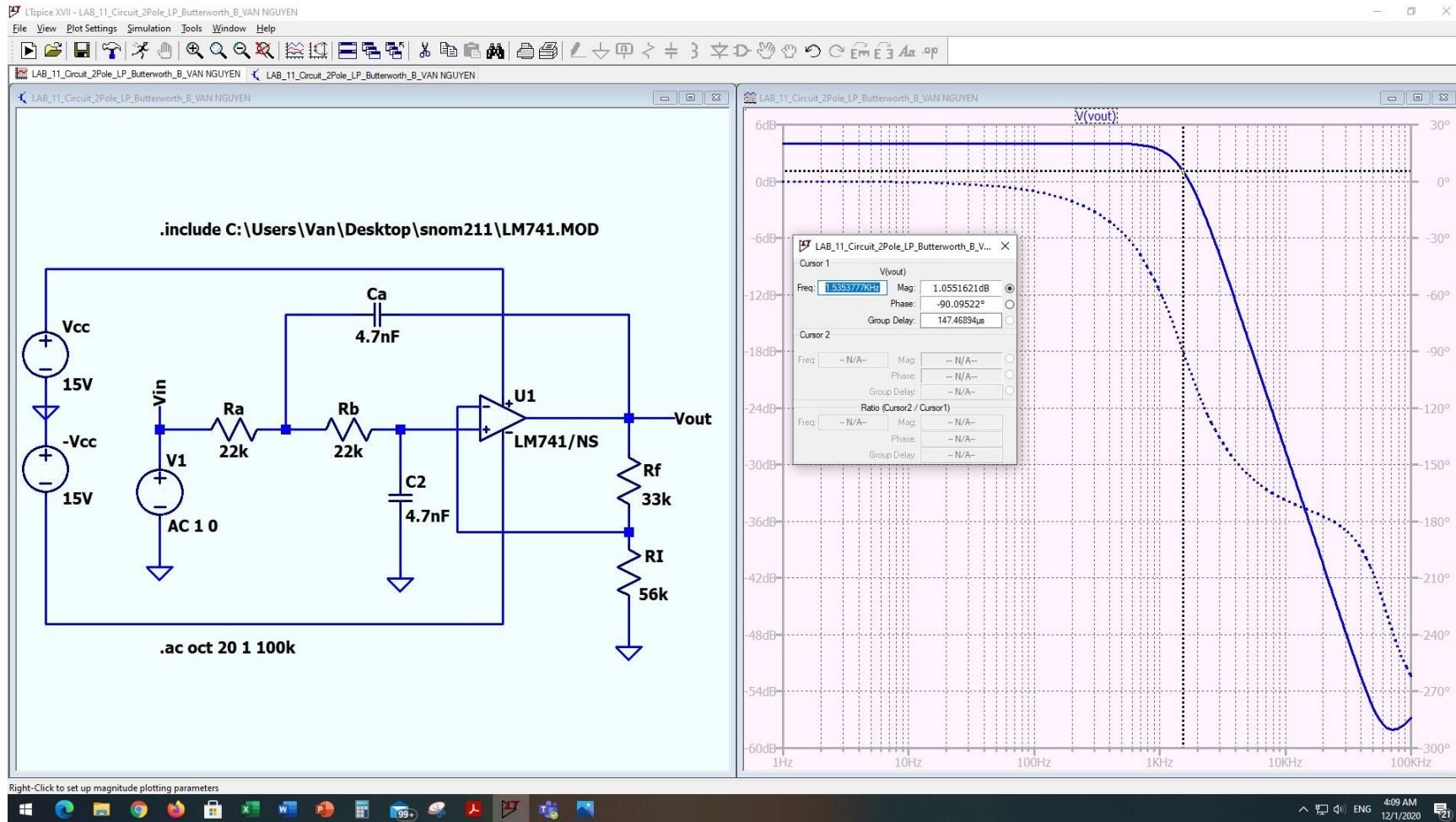1) Lab_circuit_2Pole_LP_Butterworth_A_LM741 ($f_c = 1.535 \text{ kHz}$)



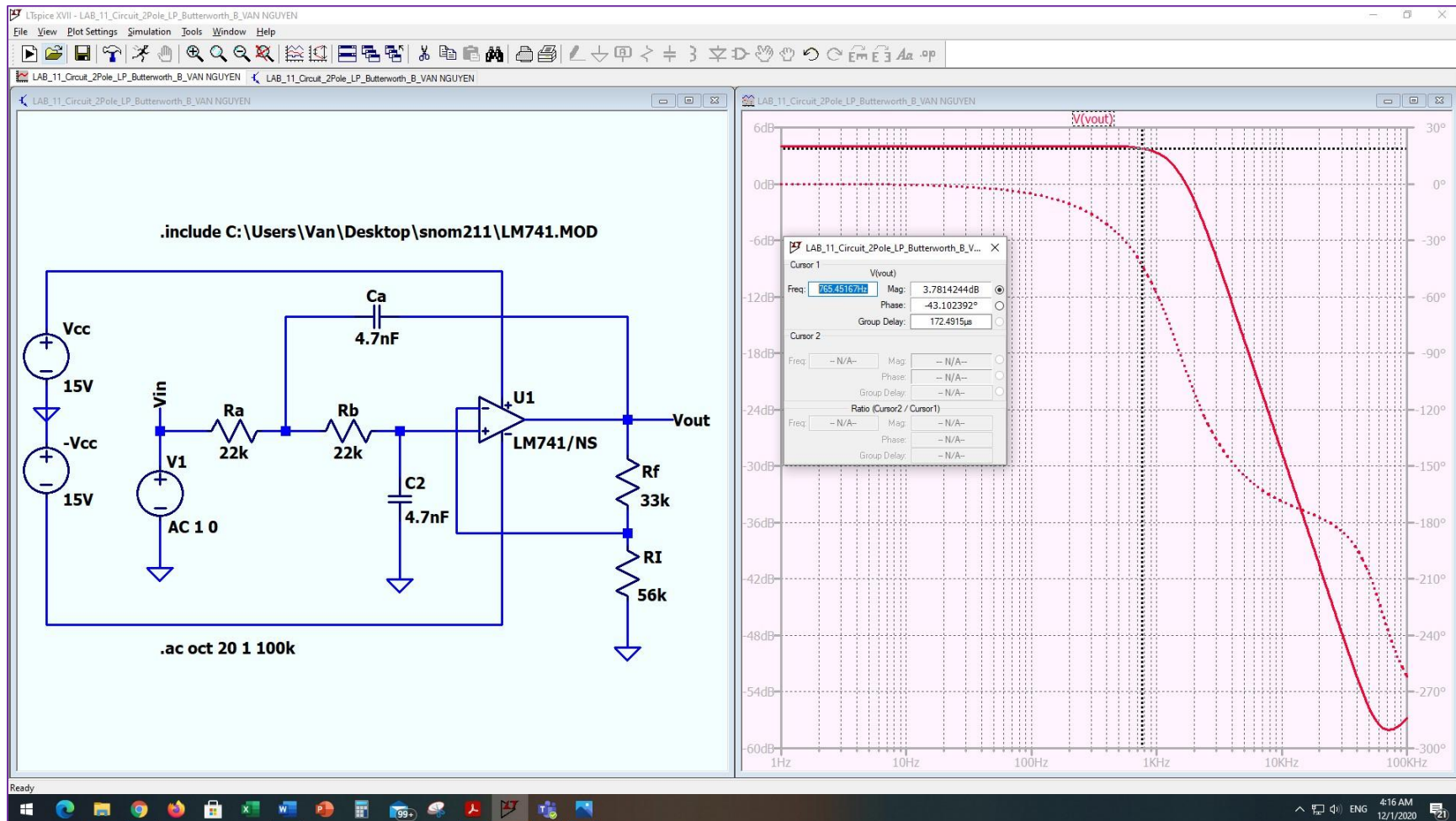2)- Lab_circuit_2Pole_LP_Butterworth_B_LM741

Half f_c values = 765 Hz. Bandwidth is measured between the 0.707 current amplitude points.



Part-2: Low-Pass Filtering of Noisy Signal

Generate a heterogeneous signal mixture for Low-Pass filtering

- Use your previous Summing Amplifier to make an arbitrary signal generator.
- Arbitrary Signal Generate can produce arbitrary mixture signal by using multiple sinusoids with different amplitudes, frequency, and phases.
- Let your arbitrary signal generator make a composite waveform by using the following three input component signals;
 - $V_{in1} = 1V_p$ sine wave with 1 kHz frequency and zero-degree phase shift
 - $V_{in2} = 1V_p$ sine wave with 10 kHz frequency and zero-degree phase shift
 - $V_{in3} = 1V_p$ sine wave with 20 kHz frequency and zero-degree phase shift

Simulate for Transient Analysis


Verify your filter operation by simulating its waveform graph that shows the output and the input of the filter in one graph as follows:

- V_{OUT}
- V_{in} •

Edit Simulation Command for Transient Analysis (Waveform Plot) as **“.tran 0.1”**

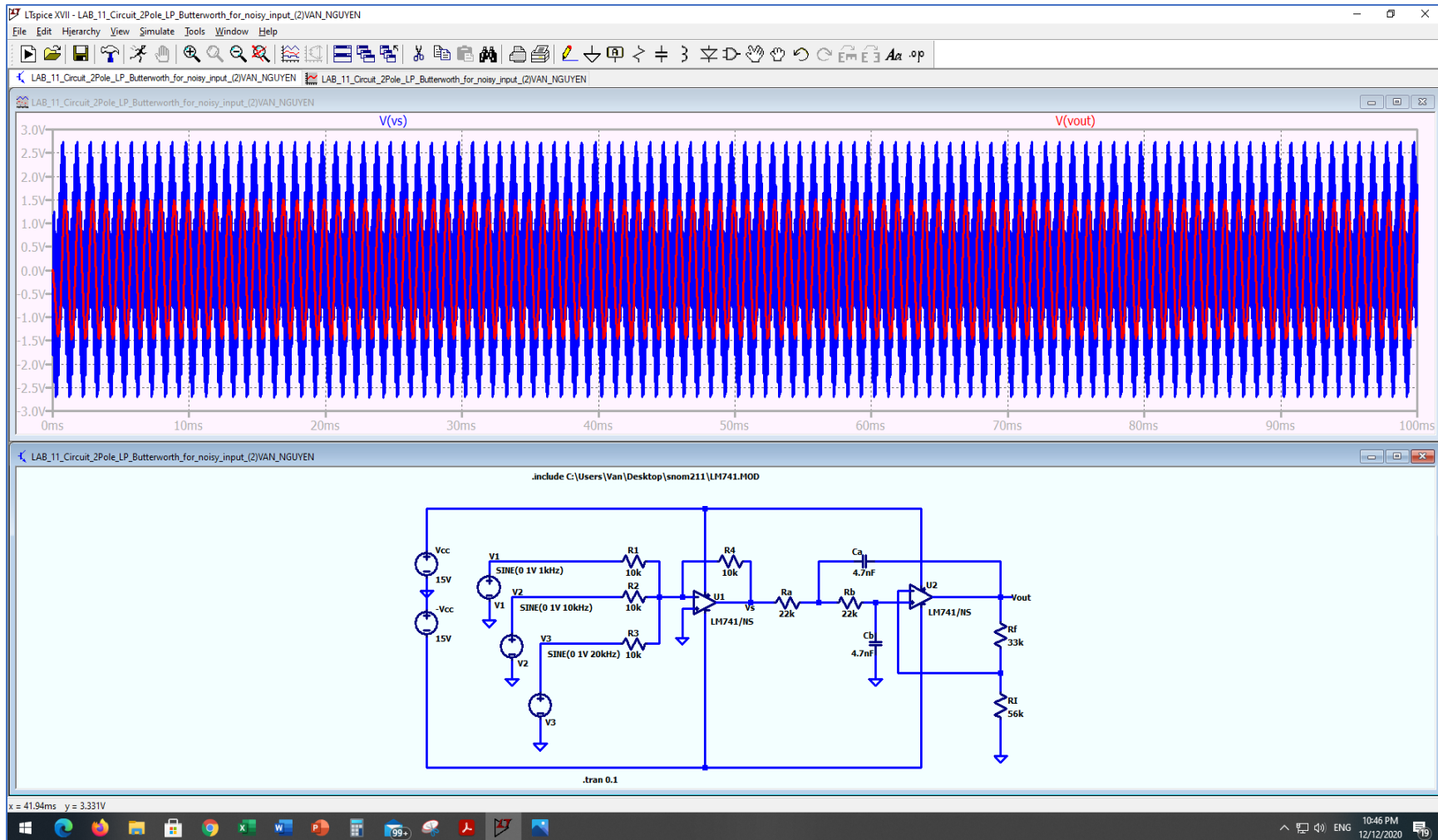
Capture the waveform graph and the schematic in one shot:



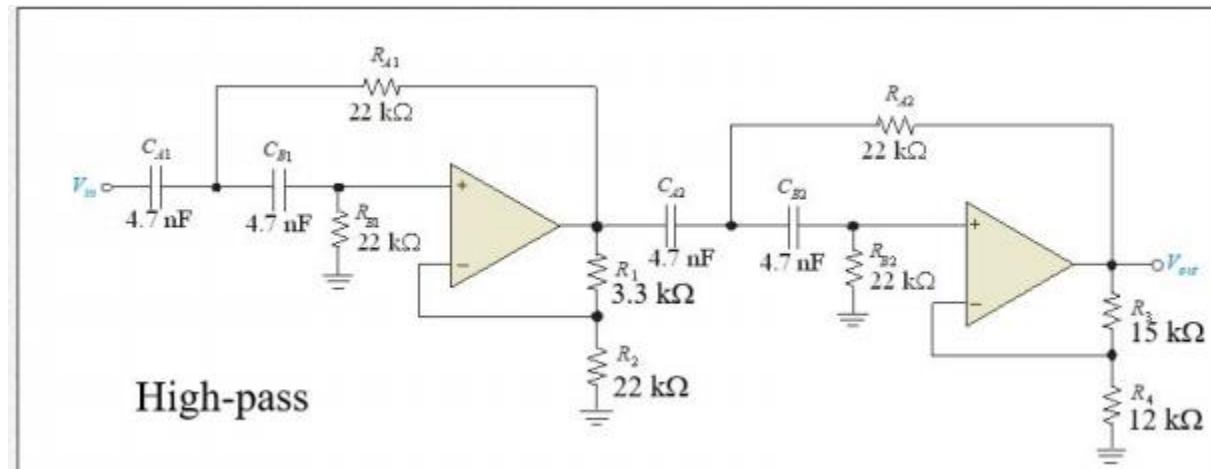
1)- Lab_simulate_2Pole_LP_Butterworth_for_noisy_input (V_{out} , V_{in} , .tran 0.1)

Part-3: High-Pass Butterworth filter

Implement 4-pole High-Pass Butterworth filter:



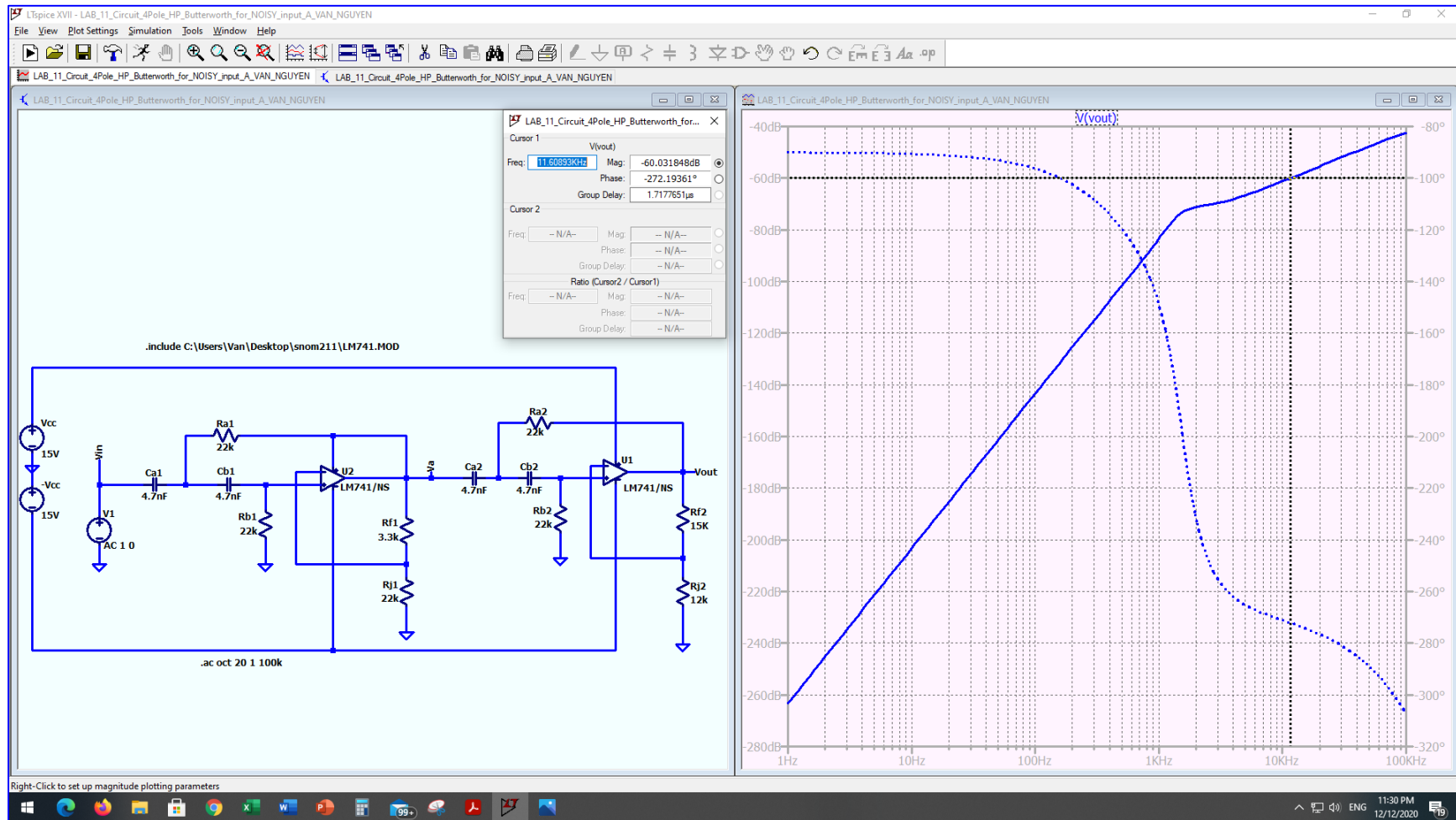- Lab_circuit_4Pole_HP_Butterworth_A; Measure critical frequency by simulation $f_c = 11.6 \text{ kHz}$ at -60 dB



Part-4: High-Pass Filtering of Noisy Signal

Generate a heterogeneous signal mixture for High-Pass filtering

You will modify the input signal mixture as follows.

Use your previous Summing Amplifier to make an arbitrary signal generator.

Arbitrary Signal Generate can produce arbitrary mixture signal by using multiple sinusoids with different amplitudes, frequency, and phases

Let your arbitrary signal generator make a composite waveform by using the following three input component signals;


- V_{in1} = 1Vp sine wave with 10 Hz frequency and zero-degree phase shift
- V_{in2} = 1Vp sine wave with 100 Hz frequency and zero-degree phase shift
- V_{in3} = 1Vp sine wave with 2 kHz frequency and zero-degree phase shift

Simulate for Transient Analysis Verify your arbitrary signal generator by simulating its waveform graph that shows the output and the three inputs in one graph as follows:

- V_{OUT}
- V_{in1}
- V_{in2}
- V_{in3}

Capture the waveform graph and the schematic in one shot, and save it as

Lab_Circuit_4POLE_HP_Butterworth_for_noisy_input (With V₁, V₂, V₂ and V_{out})

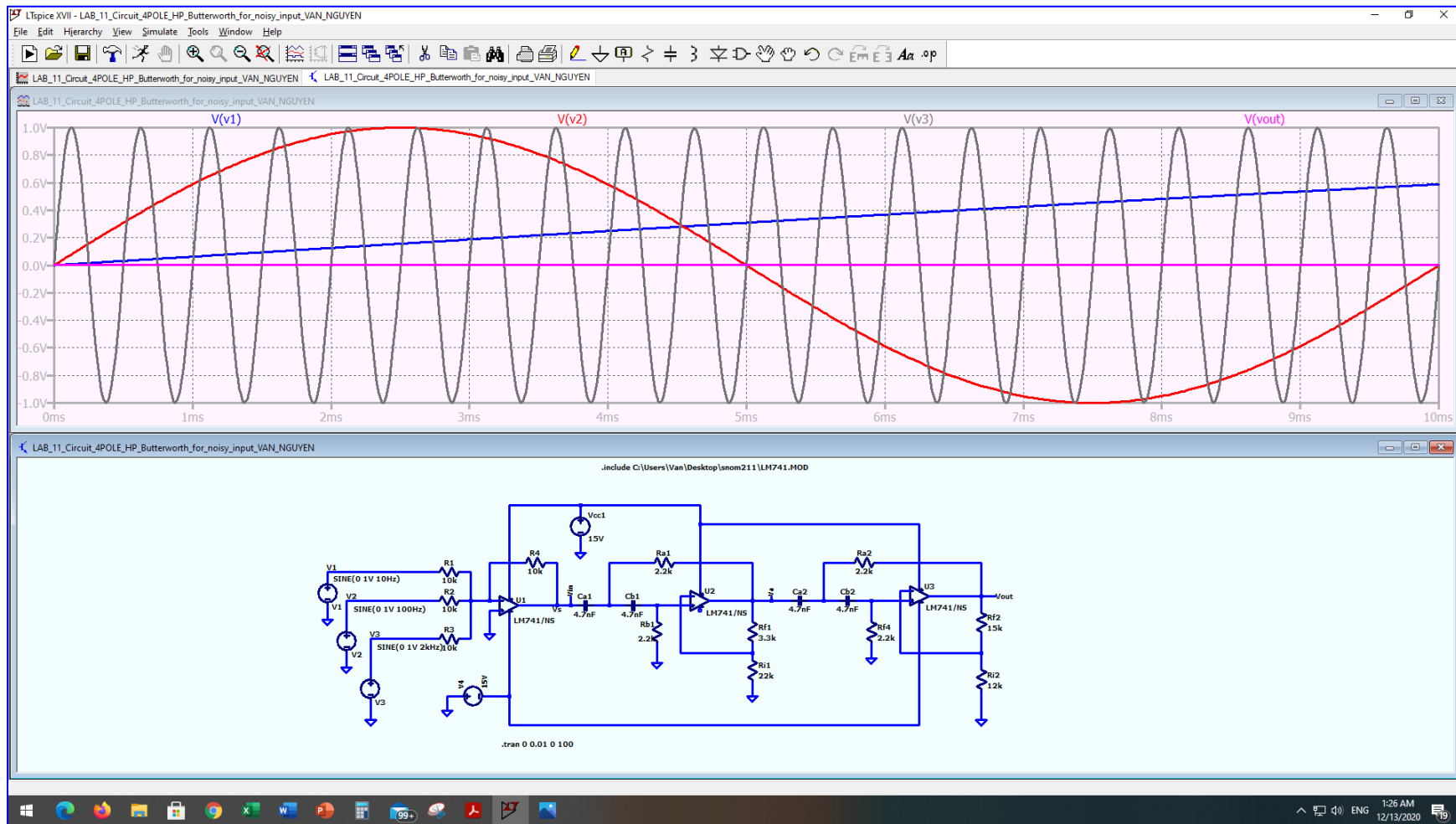

Apply 4-Pole High-pass Butterworth Filter

Use your 4-pole High-Pass Butterworth filter to pass only the highest-frequency signal component and stop the remaining signal components.

Connect the arbitrary signal generator output to the input of your lowpass filter.

Simulate for Transient Analysis


Verify your filter operation by simulating its waveform graph that shows the output and the input of the filter in one graph as follows:

- V_{OUT}
- V_{in}

Edit Simulation Command for Transient Analysis (Waveform Plot) as **“.tran 0.01”**

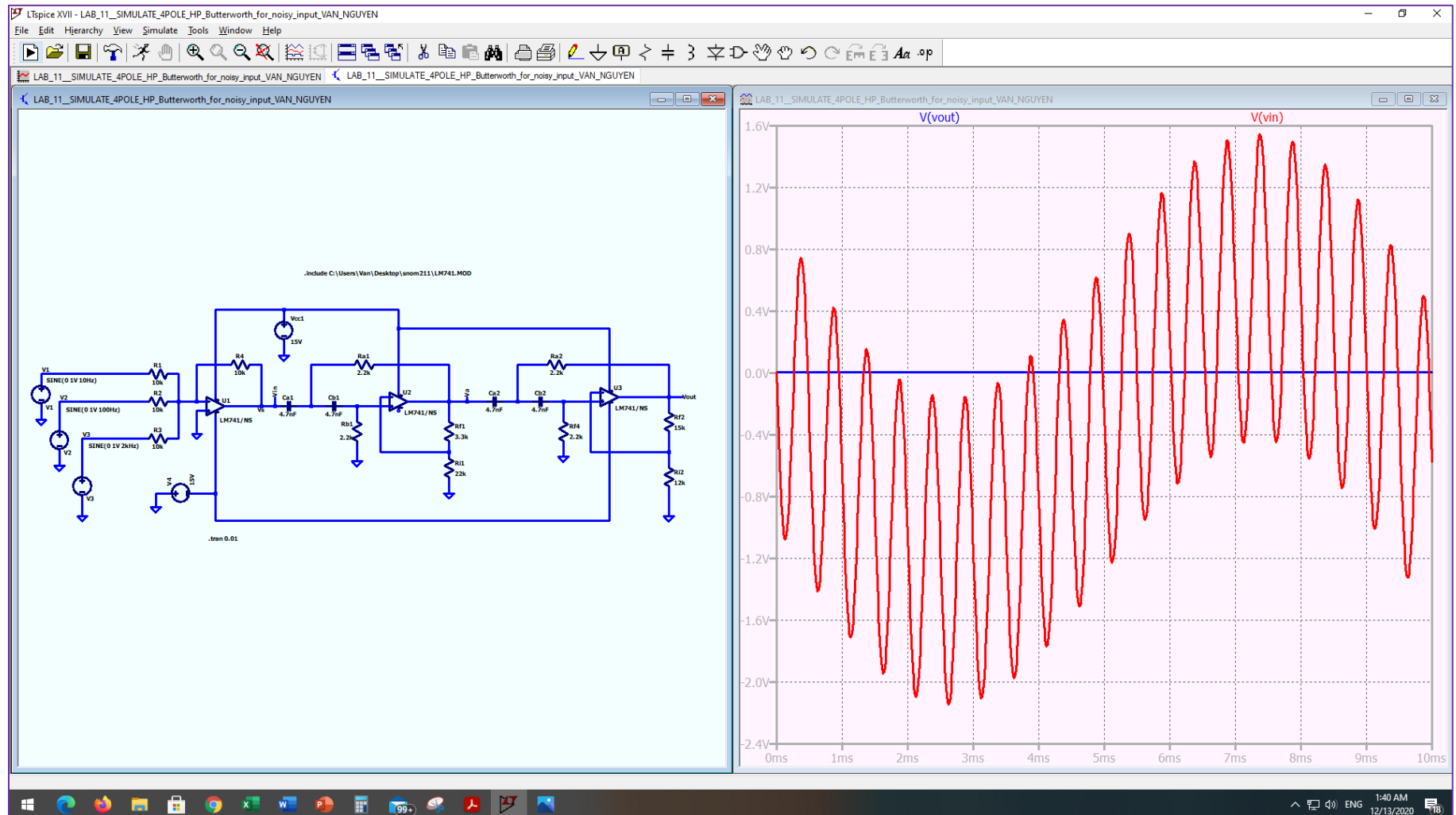Capture the waveform graph and the schematic in one shot:



Lab_Simulate_4Pole_HP_Butterworth_for_noisy_input (With Vout, Vin and “.tran 0.01”)

Lab_Simulate_HP_Butterworth_for_noisy_input_2Pole & 4Pole (With V_{out} , V_{in})

